

Computer Architecture and Organization 2020
Question and Answers

Student ID: 91815855E109


Student Name(in English): Miracle

Student Name(in Chinese): 奇迹

- **Summary of my work**

The first problem I encountered was downloading the software. Getting to the website page, there were a lot of files that looked like the right one, so I decided to watch a YouTube video to find the right one to download(even that was difficult too).

After downloading the software I read the Lab instruction which says that I should create a new project and call it alu and also add it to a location. When I got to the instruction of a working directory I was a little bit confused as to what the instruction meant by creating a working directory until I actually launched the software and followed does instructions. The instruction also said that I should add the following properties in the project settings: Spartan3E, XC3S500E,FG320,Speed of -4, Synthesis tool XST(VHDL/Verilog) Simulator:Ism(VHDL/Verilog), and preferred Language : Verilog.

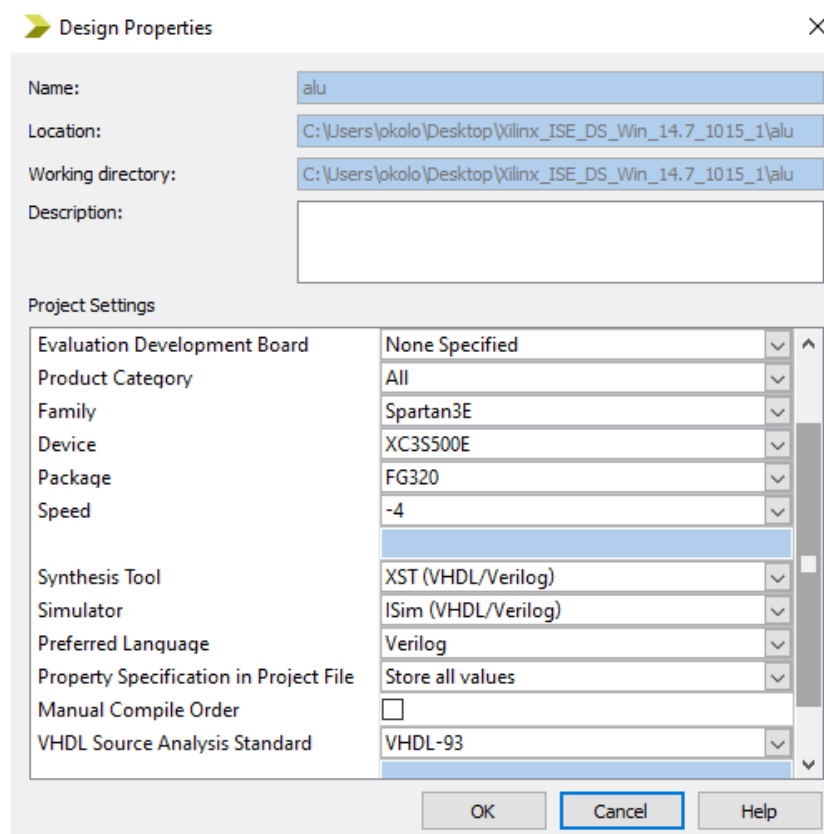

The picture of the properties


I was then instructed to create a new source file to named add1b.sch of which I did. After this instruction, came the challenge of understanding how to implement the following logic:

$$r = ci \cdot \bar{a} \cdot \bar{b} + \bar{ci} \cdot a \cdot \bar{b} + \bar{ci} \cdot \bar{a} \cdot b + ci \cdot a \cdot b$$

$$co = ci \cdot a + ci \cdot b + a \cdot b$$



Where a and b were inputs to the adder, ci was the carry-in, r was the result, and co was the carry-out. Following the requirements that were given to me, it took a lot of time to process what I was meant to do. After lots of research from the internet I realized that what I was expected to implement was a 1-bit adder of which I did:

 The specific instruction was to do this using logic gates.



My Schematic design for 1-bit adder.

 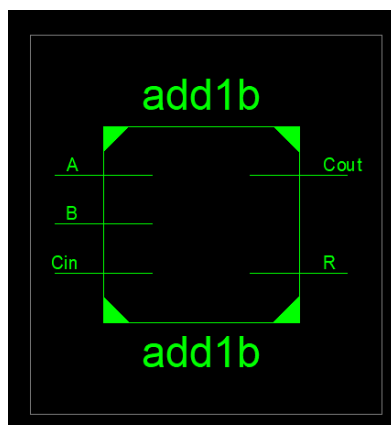
Then I was told to Synthesize my design to correct any errors. The RTL schematic is shown below: When you left-double click it looks like the picture on the right.



Next part of the lab was to create a test bench this part required me to understand verilog and vhdl programming .


This part will be further discussed in the next section.

 I was told to create a schematic symbol for my add1b.sch of which I did.




The Diagram of Schematic symbol.

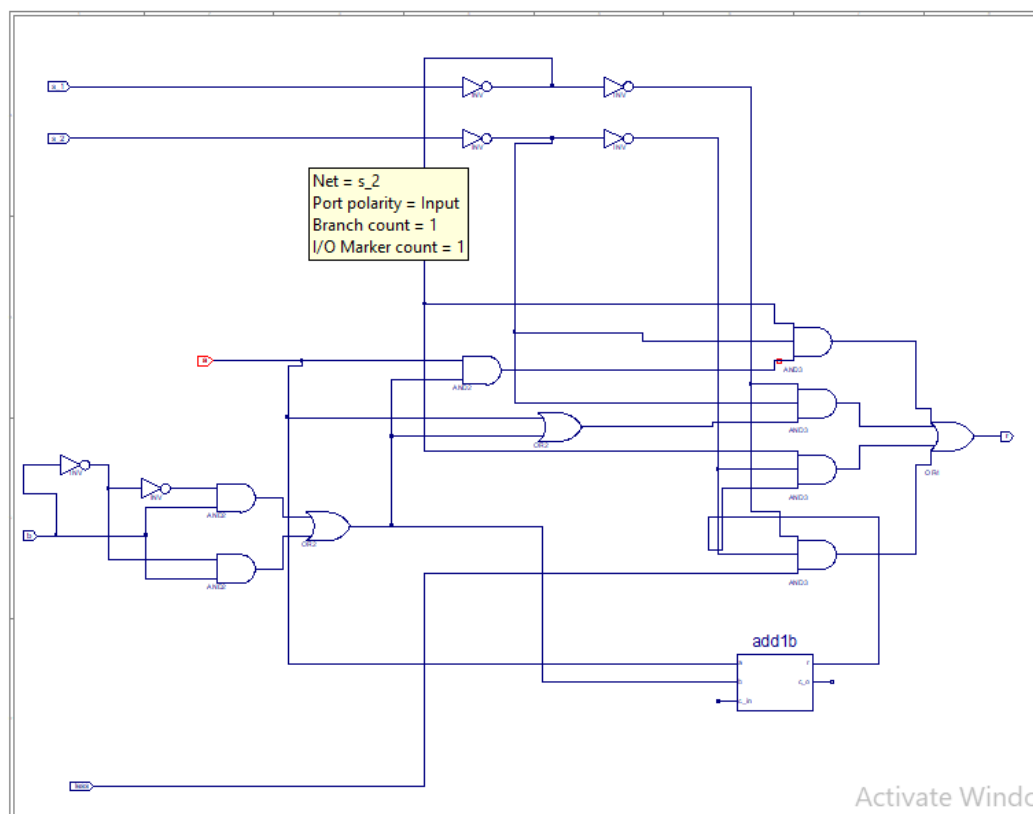Using this schematic symbol I was to implement a 1-bit ALU which I did but this required the use of a 2 to 1 multiplexer connected to b input and selector as b-inverted for the subtraction aspect of my ALU and a 4 to 1 multiplexer for selecting which operation to be done.




Initial Schematic of the 1-bit ALU

 
But as you can see it looks needlessly complicated, untidy and also not visible so I decided to create schematic symbols for each multiplexer. I created a new source file for each schematic. For the 2 to 1 multiplexer I called mux2to1 and for the 4 to 1 multiplexer I called it mux4to1 as shown below:




Schematic of 2 to 1 Multiplexer

 

Schematic Symbol of 2 to 1 multiplexer

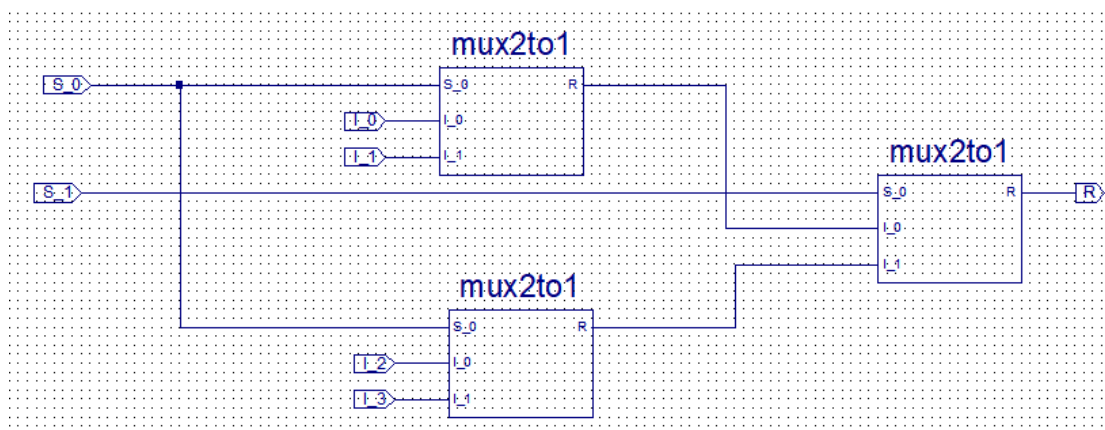


Schematic of 4 to 1 multiplexer

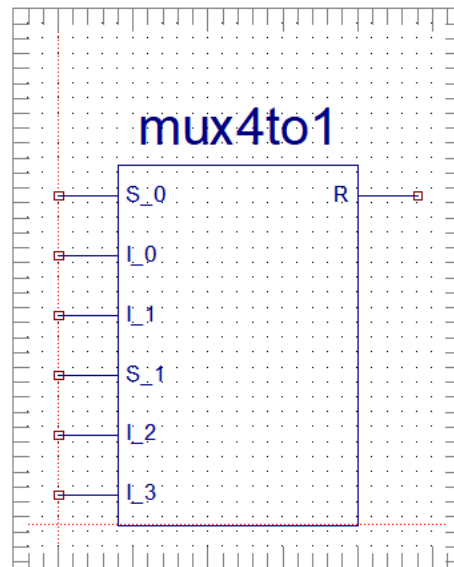


Schematic symbol of 4 to 1 multiplexer

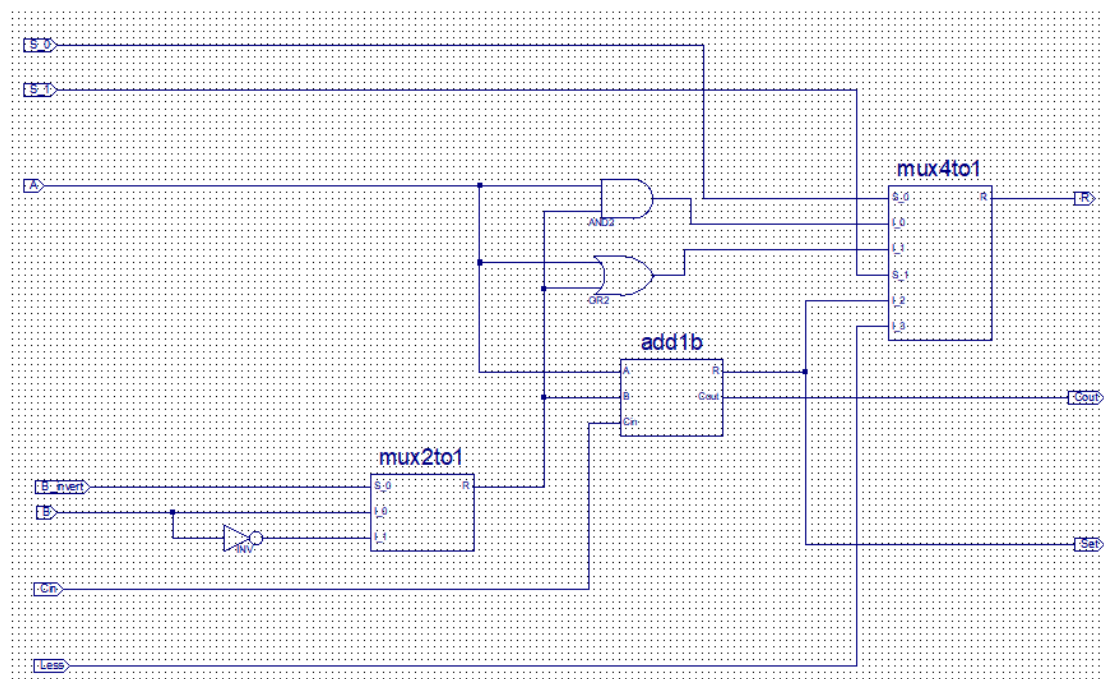From this I therefore restructured my ALU into a much tidy and less complicated Schematic. I also realized that connecting the B_invert to B was wrong because it is meant to be a selector for **Subtraction** cases. Less is used if the 4-bit A is less than the 4-bit B. Lastly, I added a set for my 4-bit alu for cases to help implement the set less than operation.



Final Schematic of the 1-bit ALU

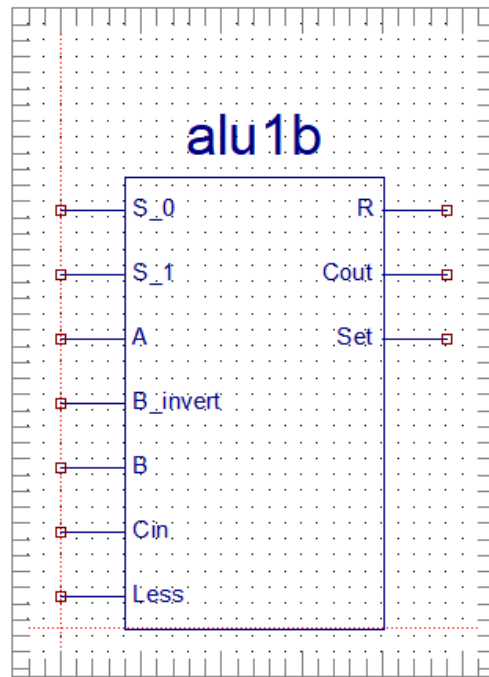

Schematic Symbol of 1-bit ALU

The test bench and Simulation will be discussed in the other sections.

- **VHDL/Verilog code**

For this section I had to do a test bench as instructed which produced the Verilog and VHDL codes of the add1b and ALU.

Add1b: Verilog

In this section the instruction said that I should replace a certain part of the verilog code form the Verilog Test Fixture to the one in the instruction manual and **also add my own code which yielded** to this:

```
`timescale 1ns / 1ps

module add1b_add1b_sch_tb();

// Inputs
reg Cin;
reg A;
reg B;

// Output
wire R;
wire Cout;

// Bidirs

// Instantiate the UUT
add1b UUT (
    .Cin(Cin),
    .A(A),
    .B(B),
    .R(R),
    .Cout(Cout)
);
// Initialize Inputs

    initial begin
        Cin = 0;
        A = 0;
        B = 0;
        #100;
        A = 1;
        B = 1;
        #200;
        A = 0;
        B = 1;

        #1;
        if((R==1)&&(Cout==0))
            $display("okay 1");
        else
            $display("fail 1");
    end
endmodule
```

VHDL

This one is gotten from the VHDL test bench.

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
LIBRARY UNISIM;
USE UNISIM.Vcomponents.ALL;
ENTITY add1b_add1b_sch_tb IS
END add1b_add1b_sch_tb;
ARCHITECTURE behavioral OF add1b_add1b_sch_tb IS

    COMPONENT add1b
    PORT( Cin      :      IN      STD_LOGIC;
          A :      IN      STD_LOGIC;
          B :      IN      STD_LOGIC;
          R :      OUT     STD_LOGIC;
          Cout     :      OUT     STD_LOGIC);
    END COMPONENT;

    SIGNAL Cin      :      STD_LOGIC;
    SIGNAL A        :      STD_LOGIC;
    SIGNAL B        :      STD_LOGIC;
    SIGNAL R        :      STD_LOGIC;
    SIGNAL Cout     :      STD_LOGIC;

BEGIN

    UUT: add1b PORT MAP(
        Cin => Cin,
        A => A,
        B => B,
        R => R,
        Cout => Cout
    );

-- *** Test Bench - User Defined Section ***
tb : PROCESS
BEGIN
    WAIT; -- will wait forever
END PROCESS;
-- *** End Test Bench - User Defined Section ***

END;
```


ALU: Verilog

I took the liberty of also displaying my code since I was asked to test bench. This result shall be shown in the Simulation section.

```
`timescale 1ns / 1ps

module alu1b_alu1b_sch_tb();

// Inputs
reg S_0;
reg S_1;
reg A;
reg B;
reg Cin;
reg Less;
reg B_invert;

// Output
wire Set;
wire Cout;
wire R;

// Bidirs

// Instantiate the UUT
alu1b UUT (
    .Set(Set),
    .S_0(S_0),
    .S_1(S_1),
    .A(A),
    .B(B),
    .Cin(Cin),
    .Less(Less),
    .B_invert(B_invert),
    .Cout(Cout),
    .R(R)
);

// Initialize Inputs

initial begin
    S_0 = 0;
    S_1 = 0;
    A = 0;
    B = 0;
    Cin = 0;
    Less = 0;
    B_invert = 0;
    //AND operation
    #100;
    S_0 = 0;
    S_1 = 0;
    A = 1;
    B = 1;
    Cin = 0;
    Less = 0;
    B_invert = 0;
    //OR operation
    #200;
    S_0 = 1;
    S_1 = 0;
    A = 0;
    B = 1;
end
```

```
Cin = 0;
Less = 0;
B_invert = 0;
//ADD operation
#300;
S_0 = 0;
S_1 = 1;
A = 0;
B = 1;
Cin = 0;
Less = 1;
B_invert = 1;
//Subtract operation
#400;
S_0 = 0;
S_1 = 0;
A = 1;
B = 1;
Cin = 1;
Less = 0;
B_invert = 1;
```

```
end
endmodule
```

VHDL

This is the Vhdl code also from the test bench.

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
LIBRARY UNISIM;
USE UNISIM.Vcomponents.ALL;
ENTITY alu1b_alu1b_sch_tb IS
END alu1b_alu1b_sch_tb;
ARCHITECTURE behavioral OF alu1b_alu1b_sch_tb IS
```

```
    COMPONENT alu1b
    PORT( Set      :      OUT   STD_LOGIC;
          S_0      :      IN    STD_LOGIC;
          S_1      :      IN    STD_LOGIC;
          A :      IN    STD_LOGIC;
          B :      IN    STD_LOGIC;
          Cin      :      IN    STD_LOGIC;
          Less     :      IN    STD_LOGIC;
          B_invert :      IN    STD_LOGIC;
          Cout     :      OUT   STD_LOGIC;
          R :      OUT   STD_LOGIC);
    END COMPONENT;
```

```
    SIGNAL Set      :      STD_LOGIC;
    SIGNAL S_0      :      STD_LOGIC;
    SIGNAL S_1      :      STD_LOGIC;
    SIGNAL A        :      STD_LOGIC;
    SIGNAL B        :      STD_LOGIC;
    SIGNAL Cin      :      STD_LOGIC;
    SIGNAL Less     :      STD_LOGIC;
    SIGNAL B_invert :      STD_LOGIC;
    SIGNAL Cout     :      STD_LOGIC;
    SIGNAL R        :      STD_LOGIC;
```

```
BEGIN
```

```
    UUT: alu1b PORT MAP(
        Set => Set,
        S_0 => S_0,
        S_1 => S_1,
        A => A,
        B => B,
        Cin => Cin,
        Less => Less,
        B_invert => B_invert,
        Cout => Cout,
        R => R
    );
```


```
-- *** Test Bench - User Defined Section ***
    tb : PROCESS
    BEGIN
        WAIT; -- will wait forever
    END PROCESS;
-- *** End Test Bench - User Defined Section ***

END;
```

● **Simulation Results**


Add1b:

 The result below is gotten from the Verilog code of the 1-bit adder



Wave form

1-bit ALU:

 

Wave form


4-bit ALU

The instruction asked for:


- Two 4-bit inputs which are A_0 to A_3 and B_0 to B_3
- 3-bit input operation which B_invert, S_0 and S_1
- 4-bit output to R_0 to R_3
- Two 1-bit output Zero and Overflow

Less and Set is not shown because they are connected to each other

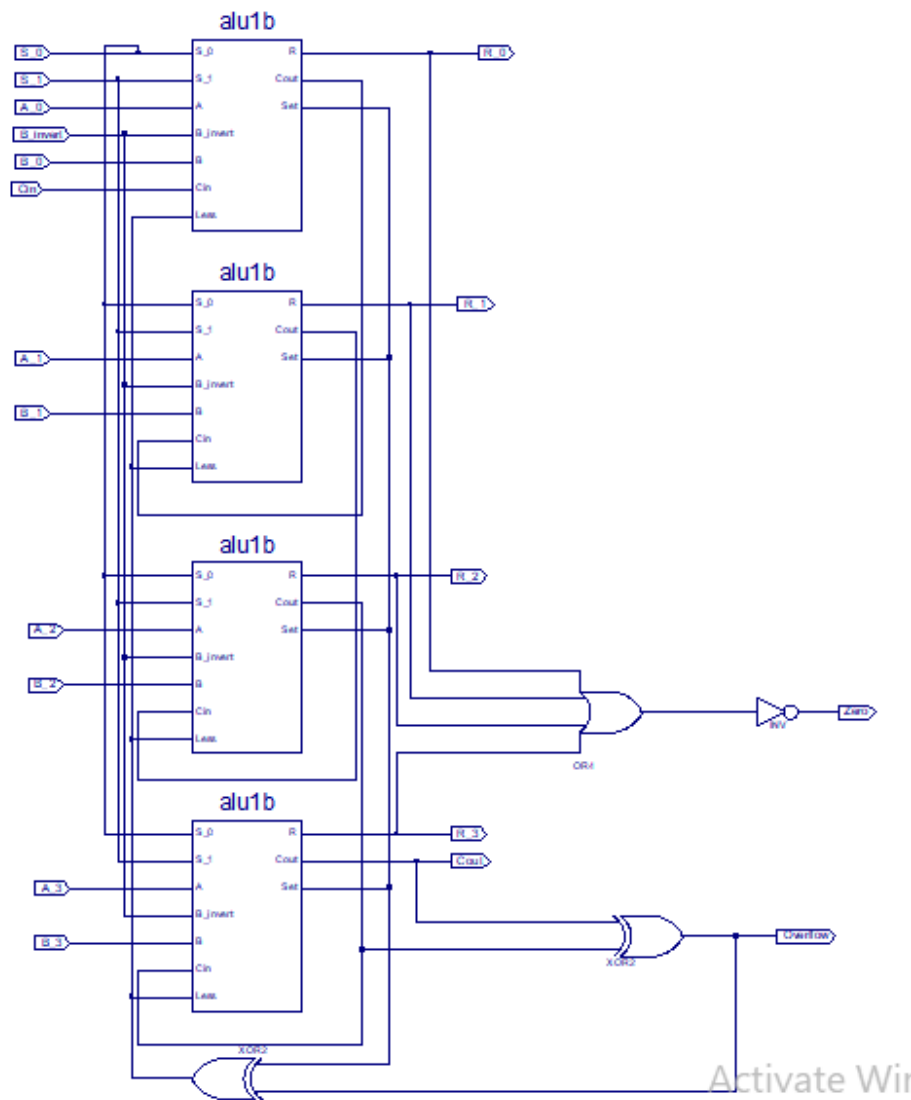Note: The Set is JOINED with Overflow in XOR and then their Output is joined with the Less.



Schematic Diagram

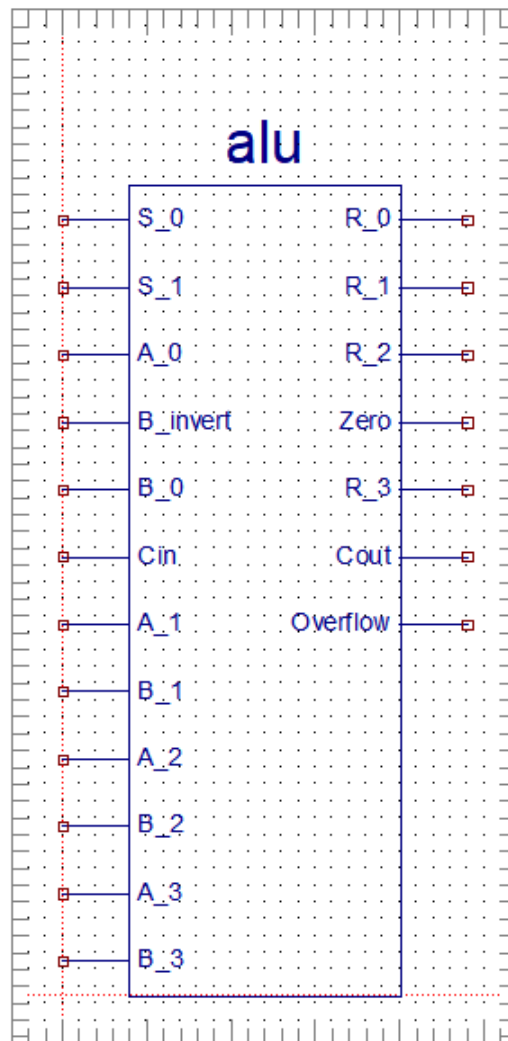


Schematic Symbol

- **Operations**

AND(000):

I shall use **A_3 = 0, A_2 = 1, A_1 = 1, A_0 = 0** and **B_3 = 1, B_2 = 1, B_1 = 1, B_0 = 0**.

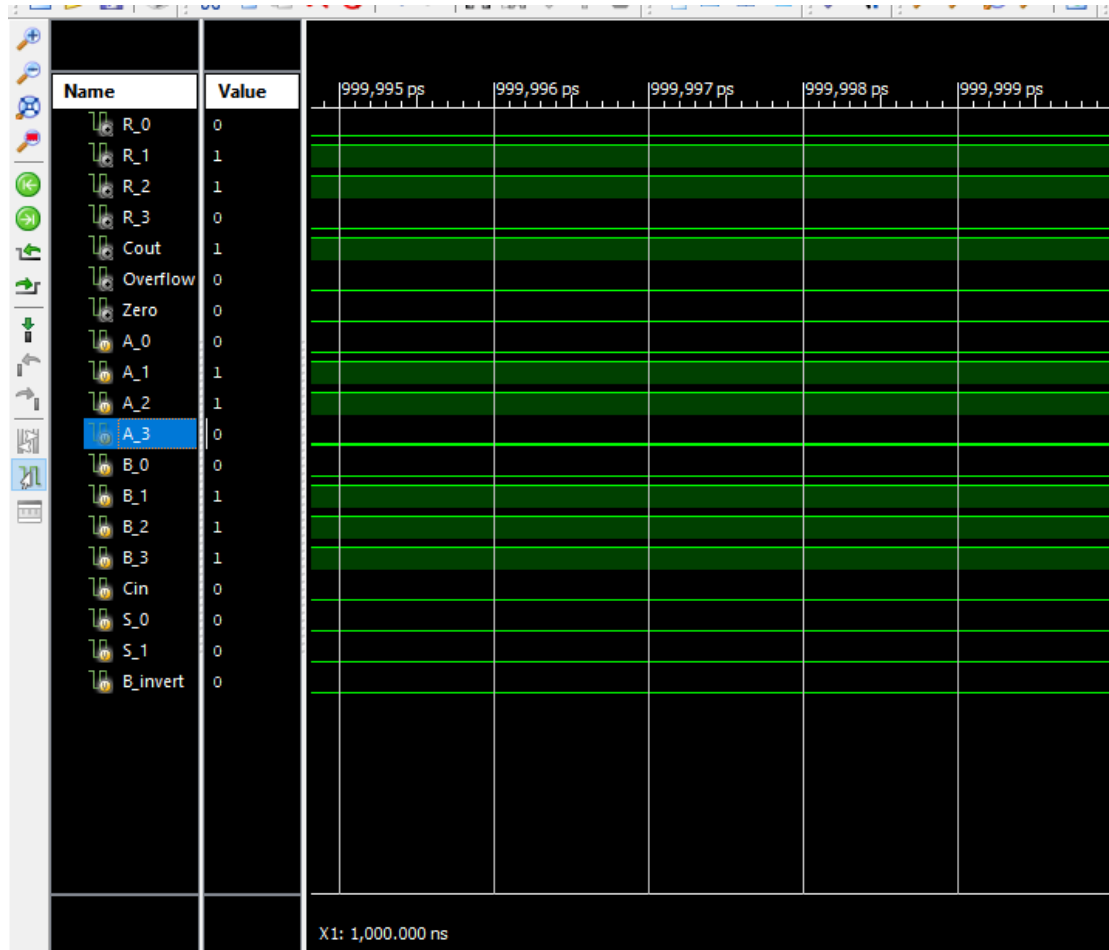This IS 0110 AND 1110 which the result is 0110.




Wave Form of Operation Result

OR(001):

I shall use $A_3 = 1, A_2 = 0, A_1 = 1, A_0 = 0$ and $B_3 = 0, B_2 = 1, B_1 = 0, B_0 = 1$.

 This IS 1010 OR 0101 which the result is 1111.




Wave Form of Operation Result

ADDITION(010):

I shall use $A_3 = 1, A_2 = 1, A_1 = 1, A_0 = 1$ and $B_3 = 0, B_2 = 1, B_1 = 1, B_0 = 1$.

 This IS 1111 ADD 0111 which the result is 0110 with Carry-out 1.




Wave Form of Operation Result

SUBTRACTION(110):

I shall use **A_3 = 1, A_2 = 0, A_1 = 1, A_0 = 1** and **B_3 = 0, B_2 = 1, B_1 = 0, B_0 = 1**.

 This IS 1011 SUBTRACT 0101 which the result is 0110. For this B_invert is equals 1 and Carry_in is equals 1.



SET LESS THAN(111): This operation is done internally. Please take a look at the Schematic.

(If A < B then Set =1 else Set =0)